



C09-AEI-304

3214

BOARD DIPLOMA EXAMINATION, (C-09)

MARCH/APRIL—2013

DAEI—THIRD SEMESTER EXAMINATION

BASIC ELECTRICAL ENGINEERING

Time : 3 hours]

[*Total Marks* : 80

PART—A

3×10=30

Instructions : (1) Answer **all** questions.

(2) Each question carries **three** marks.

(3) Answer should be brief and straight to the point and shall not exceed *five* simple sentences.

1. Define ideal voltage source.
2. State Kirchhoff's voltage law.
3. Define the terms phase and phase difference.
4. State the salient features of *j*-notation method for solving parallel circuits.
5. State the formulae for voltage, current and power factor for *R-L-C* series circuit.
6. Draw the circuit diagram of separately excited DC shunt motor.

7. Define commutation in a DC generator.
8. State torque equation of a DC motor.
9. State different cooling methods of a transformer.
10. Draw the salient pole-type rotor of an alternator.

PART—B

10×5=50

Instructions : (1) Answer *any five* questions.

(2) Each question carries **ten** marks.

(3) Answers should be comprehensive and criterion for valuation is the content but not the length of the answer.

11. (a) State Thevenin's theorem.
(b) State Norton's theorem.
12. A network of resistances, if formed as follows :
 $AB = 9$ ohms, $BC = 1$ ohm, $CA = 1.5$ ohms forming a delta and $AD = 6$ ohms, $BD = 4$ ohms, $CD = 3$ ohms forming a star internally in delta. Compute the network resistance as measured between—
 - (a) A and B
 - (b) B and C
 - (c) C and A
13. A coil of resistance 100 and inductance 100 H is connected with a 100 pF capacitor. The circuit is connected to a 10 -V variable frequency supply. Calculate the Q -factor.

- 14.** (a) Compare between series resonance and parallel resonance.
(b) Derive expression for resonant frequency in a R - L - C series circuit.
- 15.** Explain simple lap and wave windings with sketch.
- 16.** Draw and explain characteristics of a DC series generator.
- 17.** Explain the construction of core-type transformer with sketch.
- 18.** Explain the constructional features of three-phase induction motors with sketch.

★ ★ ★