



C09-AEI-304

3214

BOARD DIPLOMA EXAMINATION, (C-09)

OCT/NOV—2016

DAEI—THIRD SEMESTER EXAMINATION

BASIC ELECTRICAL ENGINEERING

Time : 3 hours]

[Total Marks : 80

PART—A

3×10=30

Instructions : (1) Answer **all** questions.
(2) Each question carries **three** marks.
(3) Answers should be brief and straight to the point and shall not exceed *five* simple sentences.

1. Write any three differences between active and passive circuits.
2. Define Thevenin's theorem.
3. Define resonance.
4. Define Q-factor.
5. Write the expression for resonance frequency in a parallel resonance circuit.
6. Define back e.m.f. in a d.c. motor and give its formula.
7. State any three losses in a d.c. machine.
8. Define efficiency and write its formula.
9. State the relation among voltage, current ratios and turns ratio in a transformer.
10. List any three applications of induction motors.


*

PART—B

10×5=50

- Instructions :** (1) Answer *any five* questions.
(2) Each question carries **ten** marks.
(3) Answers should be comprehensive and the criterion for valuation is the content but not the length of the answer.

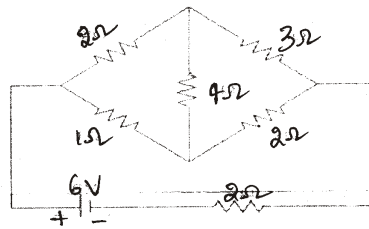11. (a) Develop transformation formula from star to delta circuit. 5
(b) Three resistances of 20 each are connected in star. Find the equivalent delta resistances. 5
12. Determine the current, voltage across 4 resistor as shown in the figure below by using Kirchhoff's voltage law :



13. Derive impedance, power and power factor in a series R-C circuit.
14. Derive relationship between voltage and current in a pure resistive circuit.
15. Explain construction of d.c. machine along with a diagram.
16. Explain electrical and mechanical characteristics of d.c. series motors.
17. Explain construction and working of transformer along with a diagram.
18. List the constructional features of the following : 5×2=10
(a) Salient pole alternators
(b) Non-salient pole alternators
