



C09-AEI-304

3214

BOARD DIPLOMA EXAMINATION, (C-09)

MARCH/APRIL—2017

DAEI—THIRD SEMESTER EXAMINATION

BASIC ELECTRICAL ENGINEERING

Time : 3 hours]

[Total Marks : 80

PART—A

3×10=30

Instructions : (1) Answer **all** questions.
(2) Each question carries **three** marks.
(3) Answers should be brief and straight to the point and shall not exceed *five* simple sentences.


1. Define junction and loop.
2. State maximum power transfer theorem.
3. Write any three differences between series and parallel resonance.
4. Draw circuit diagram of parallel resonance circuits.
5. Write the expression for resonance frequency in a series resonance circuit.
6. Define 'commutation' in a DC machine.
7. State the e.m.f equation of a DC generator and indicate the terms involved in it.
8. Mention the principle on which DC motor works.
9. Define autotransformer.
10. State the e.m.f. equation of an alternator and indicate the terms involved in it.

PART—B

10×5=50

- Instructions :** (1) Answer *any five* questions.
(2) Each question carries **ten** marks.
(3) Answers should be comprehensive and the criterion for valuation is the content but not the length of the answer.

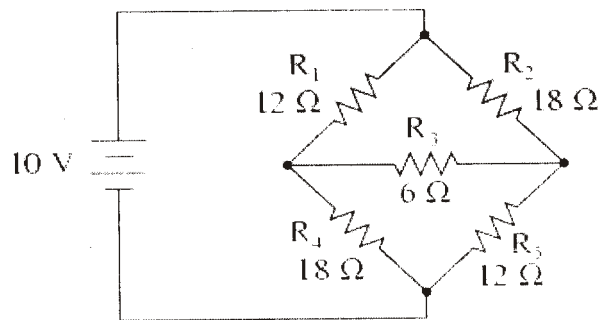11. (a) Explain ideal voltage source and ideal current source. 6
(b) State superposition theorem. 4
12. Find the resistance between the terminals of the battery in bridge network using star-delta transformation and the total current flowing in the circuit as shown in the figure :



13. Derive the relationship between voltage and current in a pure capacitive circuit.
14. Derive impedance, current and phase angle in a series R - L circuit.
15. Classify DC machines with reference to excitation and write the formulae for the above classification.
16. Explain the electrical and mechanical characteristics of DC compound motors.
17. Explain any two methods of cooling a transformer.
18. (a) Explain the constructional features of single-phase induction motor. 5
(b) Explain the principle of working of synchronous motors. 5
