



C09-AEI-305

3215

BOARD DIPLOMA EXAMINATION, (C-09)

OCT / NOV-2015

DAEI - THIRD SEMESTER EXAMINATION

DIGITAL ELECTRONICS

Time : 3 hours]

[Total Marks : 80

PART - A

3 X 10 = 30

Instructions : (1) Answer **all** questions.
(2) Each question carries **three** marks.
(3) Answers should be brief and straight to the point and shall not exceed *five* simple sentences.

1. Draw the symbols and truth tables for AND and OR gates.
2. State any two postulates of Boolean algebra.
3. Draw full adder using two half adders and OR gate.
4. Draw the block diagram of serial-adder.
5. State the need for preset and clear inputs.
6. Draw T flip-flop with truth table.
7. Draw 3-bit asynchronous counter.
8. List the types of data transfer in register.
9. List the numbers of different RAM ICs.
10. State the need for an A/D conversion.

/3215

1

[Contd...

*

PART - B

10 X 5 = 50

Instructions : (1) Answer *any five* questions.

(2) Each question carries **ten** marks.

(3) Answers should be comprehensive and the criterion for valuation is the content but not the length of the answer.

11. (a) Develop AND, OR and NOT operations using NAND gates.
(b) Simplify the expression $f = A\bar{B}\bar{C} + \bar{A}BC + A\bar{B}C + \bar{A}\bar{B}C$ using K-map.
12. Perform binary addition, subtraction, multiplication and division for 1011.11 and 1001.01.
13. (a) Draw and explain the 4×1 multiplexer circuit with truth table.
(b) Differentiate between series adder and parallel adder in any three aspects.
14. a) Explain the working of 4 to 2 encoder with truth table.
b) State the need for tri-state buffer.
15. Explain 5-bit asynchronous up/down counter with truth table.
16. (a) Draw and explain SR flip-flop using NAND gates.
(b) Differentiate between synchronous SLC and asynchronous SLC.
17. (a) Draw and explain the working of ring counter.
(b) List any three applications of ring counter.
18. Explain D/A conversion using weighted resistors.

*

* * *

*