



C14-AEI-303

4216

BOARD DIPLOMA EXAMINATION, (C-14)

OCT/NOV—2016

DAEI—THIRD SEMESTER EXAMINATION

ELECTRONIC DEVICES AND APPLICATIONS

Time : 3 hours]

[Total Marks : 80

PART—A

3×10=30

Instructions : (1) Answer **all** questions.

(2) Each question carries **three** marks.

(3) Answers should be brief and straight to the point and shall not exceed *five* simple sentences.

1. Sketch the energy level diagrams for conductors, insulators and semiconductors.

2. List any three applications of *P-N* junction diode.

3. Classify filters.

4. Draw the construction symbol and circuit symbol of a *P-N-P* transistor.

5. Draw the common collector transistor configuration.

6. List any three advantages of JFET over BJT.

7. List the types of MOSFET.

- * 8. Sketch the ISI circuit symbols of TRIAC, DIAC and GTO SCR.
- 9. Draw the light dimmer circuit using DIAC and TRIAC.
- 10. List any three applications of operational amplifier.

PART—B

10×5=50

Instructions : (1) Answer *any five* questions.

(2) Each question carries **ten** marks.

(3) Answers should be comprehensive and the criterion for valuation is the content but not the length of the answer.

- 11. Describe the working of a *P-N* junction diode with various biasing voltages and sketch its forward and reverse voltage characteristics.
- 12. Draw and explain the working of clipper and clamper circuits using diodes.
- 13. (a) Distinguish between Zener breakdown and Avalanche breakdown. 5
 (b) Write any five comparisons between IC and discrete component circuit. 5
- 14. Describe the working of a transistor as an amplifier with a circuit diagram.
- 15. Derive the relationship among alpha, beta and gamma factors.
- 16. Explain the construction and working of *n*-channel JFET and draw its drain characteristics.
- * 17. Explain the construction and working of a DIAC and draw its volt-ampere characteristics under forward bias and reverse bias.
- 18. Draw and explain the battery charger circuit using SCR.
