



C14-AEI-303

4216

BOARD DIPLOMA EXAMINATION, (C-14)

OCT/NOV—2017

DAEI—THIRD SEMESTER EXAMINATION

ELECTRONIC DEVICES AND APPLICATIONS

Time : 3 hours]

[Total Marks : 80

PART—A

3×10=30

Instructions : (1) Answer **all** questions.

(2) Each question carries **three** marks.

(3) Answers should be brief and straight to the point and shall not exceed *five* simple sentences.

1. List any three electrical properties of solid semiconductor materials.
2. List any three applications of diode.
3. State the need of filters.
4. Draw the symbols of *n-p-n* and *p-n-p* transistors.
5. Draw the CB transistor configuration.
6. List any three applications of UJT.
7. Draw the drain characteristics of JFET.
8. Draw the volt-ampere characteristics of SCR.

* 9. Draw circuit diagram of simple zener regulator.

10. List any three specifications of ICs.

PART—B

10×5=50

Instructions : (1) Answer any **five** questions.

(2) Each question carries **ten** marks.

(3) Answers should be comprehensive and the criteria for valuation are the content but not the length of the answer.

11. (a) Explain the formation of *P*-type material and sketch the energy band diagram. 5

(b) Distinguish between zener breakdown and avalanche breakdown. 5

12. Explain the working of centre-tap full wave rectifier circuit with waveforms.

13. Explain the working of *P-N-P* transistor with diagram.

14. (a) Derive the relationships between alpha and beta factors. 5

(b) Explain the working of CE transistor as an amplifier. 5

15. Explain the working principle of UJT transistor as an amplifier.

16. Explain the battery charger circuit using SCR with diagram.

17. Explain the battery charger circuit using SCR with diagram.

* 18. (a) Compare ICs with discrete component circuits. 5

(b) Give the expression for efficiency peak inverse value and ripple factor of half wave rectifier. 5
