



C14-AEI-304

4217

BOARD DIPLOMA EXAMINATION, (C-14)
OCT/NOV—2018
DAEIE—THIRD SEMESTER EXAMINATION
DIGITAL ELECTRONICS

Time : 3 hours]

[Total Marks : 80

PART—A

3×10=30

Instructions : (1) Answer **all** questions.
(2) Each question carries **three** marks.
(3) Answers should be brief and straight to the point and shall not exceed *five* simple sentences.

1. Compare between weighted and unweighted codes in any three aspects.
2. Convert $(123)_2$ into decimal and octal number systems.
3. Draw half-adder circuit using exclusive OR gate and an AND gate.
4. List any three applications of decoders.
5. Draw the diagram of T flip-flop and write its truth table.
6. List any three applications of ring counter.
7. Define modulo-N counter.
8. Draw the diagram of shift right register.

- * 9. List any three types of memory.
10. Define the terms resolution and settling time of D/A converter.

PART—B

10×5=50

Instructions : (1) Answer any **five** questions.
 (2) Each question carries **ten** marks.
 (3) Answers should be comprehensive and the criterion for valuation is the content but not the length of the answer.

11. (a) Subtract $(1101)_2$ from $(1000)_2$ using 2's complement method. 5
 (b) Simplify \overline{ABC} $\overline{A}BC$ $A\overline{B}\overline{C}$ $A\overline{B}C$ using K-map. 5
12. Explain the working of NAND and NOR gates using truth tables.
13. (a) Explain the working of 1×4 demultiplexer. 5
 (b) Draw and explain 4-bit parallel adder using full adders. 5
14. Explain two-bit digital comparator.
15. Explain J-K master-slave flip-flop with its truth table.
16. Explain asynchronous ripple counter with the help of flip-flops and draw waveforms.
- * 17. (a) Explain the basic principle of working of ROM. 5
 (b) Explain the working of serial in serial out register. 5
18. Explain D/A converter using R-2R ladder network.
