



C14-AEI-402

4414

BOARD DIPLOMA EXAMINATION, (C-14)
SEPTEMBER/OCTOBER - 2020
DAEIE—FOURTH SEMESTER EXAMINATION

NETWORK THEORY

Time : 3 hours]

[Total Marks : 80

PART—A

3×10=30

Instructions : (1) Answer **all** questions.
(2) Each question carries **three** marks.
(3) Answers should be brief and straight to the point and shall not exceed *five* simple sentences.

1. List any three differences between active and passive circuits.
2. State Kirchhoff's voltage law.
3. Define the term junctioning circuits.
4. Define co-tree and links in a circuit.
5. Define node and principal node in the circuit.
6. State Thevenin's theorem.
7. List any three advantages of maximum power transfer theorem.

- * 8. Define the term resistance.
9. Define resonance.
10. State the importance of Q -factor.

PART—B

10×5=50

Instructions : (1) Answer *any five* questions.

(2) Each question carries **ten** marks.

(3) Answers should be comprehensive and the criterion for valuation is the content but not the length of the answer.

11. Find the star equivalent circuit for the delta connected circuit shown in Fig. 1 :

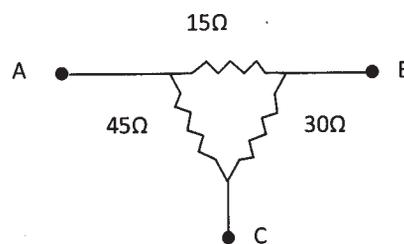


Fig. 1

12. Explain star and delta circuits with diagrams.

13. Write the mesh current equations in the circuit shown in Fig. 2 and determine the currents I_1 and I_2 :

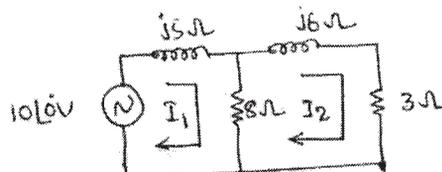


Fig. 2

- * 14. In the network shown in Fig. 3, determine V_1 and V_2 :

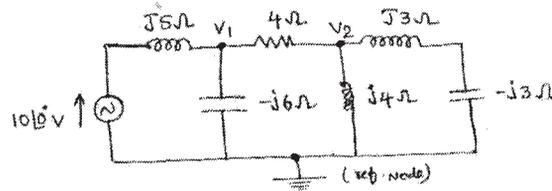


Fig. 3

15. Verify the reciprocity theorem for the network shown in Fig. 4 :

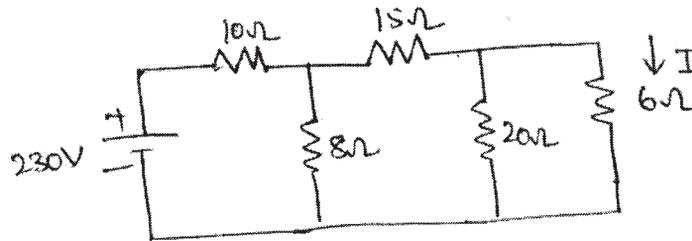


Fig. 4

16. Find the current I in the network shown in Fig. 5 using superposition theorem :

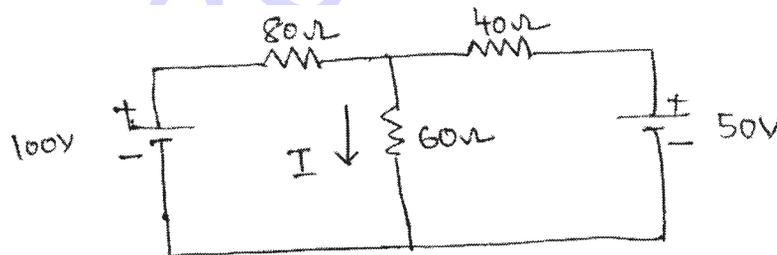


Fig. 5

17. Derive the expression for impedance, current, phase angle, power and power factor in series R - C circuits.

18. Derive the relationship between voltage and current in pure capacitive circuit.
