

*

4609
BOARD DIPLOMA EXAMINATION, (C-14)
MARCH /APRIL-2019
DAEIE - FIFTH SEMESTER EXAMINATION
LINEAR INTEGRATED CIRCUITS & APPLICATIONS

Time: 3 hours

Max. Marks: 80

PART -A**10x3=30M**

Instructions : 1) Answer **all** questions. Each question carries **three** marks
2) Answer should be brief and straight to the point and shall not exceed five simple sentences.

- 1) Define the term slew rate with reference to operational amplifier.
- 2) Give the manufacturing methods of linear IC's.
- 3) Write the formula of output voltage for differentiator circuit.
- 4) Give the applications of OP AMP in open loop operation.
- 5) List the disadvantages of active filters.
- 6) Draw the circuit of LPF using operational amplifier.
- 7) List applications of a 555 IC timer.
- 8) Give the formula for output frequency of Astable multivibrator.
- 9) Draw input, output waveforms of a schmitt trigger circuit.
- 10) List any three applications of PLL circuit.

*

*

*

PART-B

10x5=50M

Instructions : 1) Answer any **five** questions and Each question carries **ten** marks.

2) Answer should be comprehensive and criterion for valuation is the content but not the length of the answer.

- 11) Explain the integrated operational amplifier with block diagram.
- 12) Explain the operation of a differential amplifier with circuit.
- 13) Describe the operation of an Instrumentation amplifier with a circuit diagram.
- 14) Explain the operation of a voltage follower circuit and give its advantages.
- 15) Sketch the ideal and practical response plots for L.P.F, H.P.F, B.P.F, and B.S.F.
- 16) Explain the operating principle of a phase locked loop (PLL) with the help of a block diagram.
- 17) Explain the functional block diagram of a timer 555 IC. 10M
- 18) a) Explain the operation of a basic comparator circuit. 5M
b) Explain the use of a 555 IC to generate a square waveform using a diode in Astable mode. 5M

*

* * *

*