



C16-AEI-303

6215

**BOARD DIPLOMA EXAMINATION, (C-16)
OCT/NOV—2018**

DAEI-THIRD SEMESTER EXAMINATION

DIGITAL ELECTRONICS

Time : 3 hours

[Total Marks 80

PART—A

10×3=30Marks

- Instructions :** (1) Answer **all** questions.
(2) Each question carries **three** marks.
(3) Answers should be brief and straight to the point and shall not exceed **five** simple sentences.

1. Compare weighted and un-weighted codes.
2. State De-Morgan theorems.
3. List the applications of encoders.
4. Draw the 4 bit parallel adder using full adders.
5. State the need of 'present' and 'clear' inputs.
6. Draw the diagram of decade counter.
7. Draw the diagram of D flip-flop with truth table.
8. List various types of memories.
9. State the need of a register.
10. State the need of A/D converter.

PART—B

- * **Instructions :** (1) Answer any **five** questions.
(2) Each question carries **ten** marks.
(3) Answers should be comprehensive and the criterion for valuation is the content but not the length of the answer.
- 11.** Reduce the expression using Boolean laws $ABC + ABC + ABC + ABC + ABC + ABC + ABC + ABC$ and draw the gate diagrams for original and reduced expressions.
- 12.** a) Explain the working of exclusive-Or gate with truth table.
b) State the use of alphanumeric codes in ASCII and EBCDI.
- 13.** Explain 2's complement adder - subtracter with diagram.
- 14.** Explain 4×1 multiplexer with truth table and list the applications.
- 15.** Explain asynchronous ripple counter (MOD-16) with flip-flops and timing diagrams.
- 16.** Explain master slave JK flip flop with truth table and diagram.
- 17.** Explain the working of serial in serial out, parallel in serial out, serial in parallel out and parallel in parallel out registers with diagrams.
- 18.** Explain D/A conversion using counter method with diagram.