# C16-AEI-304

# 6216

### **BOARD DIPLOMA EXAMINATION, (C-16)**

#### AUGUST/SEPTEMBER—2021

### DAEI - THIRD SEMESTER EXAMINATION

#### ELECTRONIC MEASURING INSTRUMENTS

Time: 3 hours ]

PART—A

[ Total Marks : 80

3×10=30

- **Instructions**: (1) Answer **all** questions.
  - (2) Each question carries three marks.
  - (3) Answers should be brief and straight to the point and shall not exceed five simple sentences.
  - **1.** Classify bridge circuits based on exciting voltage and mention the balancing conditions of bridges.
  - **2.** State the principle of rectifier type voltmeter.
  - **3.** Draw the circuit diagram of shunt type ohmmeter.
  - **4.** List the specifications of digital multimeter.
  - **5.** Draw the diagram of ramp type digital voltmeter.
  - 6. State the necessity of time base generator.
  - **7.** State the conditions for flicker-free waveforms.
  - **8.** List any three specifications of CRO.
  - **9.** List the applications of RF signal generator.
  - **10.** State the necessity of plotter.

### /6216

[ Contd...

## PART—B

#### **Instructions :** (1) Answer *any* **five** questions.

- (2) Each question carries **ten** marks.
- (3) Answers should be comprehensive and criterion for valuation is the content but not the length of the answer.
- **11.** Explain the construction and principle of operation of PMMC instrument with diagram.
- **12.** Explain the inductance measurement using Maxwell's bridge.
- **13.** Explain the working of digital LCR meter with block diagram.
- **14.** Explain the working of successive approximation type digital voltmeter with block diagram.
- **15.** Explain the block diagram of general purpose CRO.
- **16.** Explain the principle of operation of storage oscilloscope with block diagram.
- **17.** Explain the working of AF oscilloscope (sine and square) with block diagram.
- **18.** Explain the working of XY recorders with block diagram.

#### $\star \star \star$