

\*



C14-CM-302

4232

BOARD DIPLOMA EXAMINATION, (C-14)

MARCH/APRIL—2016

DCME—THIRD SEMESTER EXAMINATION

BASIC ELECTRICAL AND ELECTRONICS ENGINEERING

Time : 3 hours ]

[ Total Marks : 80

PART—A

3×10=30

**Instructions** : (1) Answer **all** questions.

(2) Each question carries **three** marks.

(3) Answers should be brief and straight to the point and shall not exceed *five* simple sentences.


1. Define (a) current, (b) EMF and (c) specific resistance.
2. Find the value of  $R_1$  and  $R_2$  when connected in series, net resistance is 10 and when connected in parallel is 20 .
3. State Kirchhoff's laws.
4. Define (a) branch, (b) loop and (c) junction in a network.
5. State Fleming's right-hand rule.
6. Define PTC and NTC of thermistor.
7. Define the term biasing in the transistor.
8. Derive the relation between and .
9. Explain a valency band and a conduction band.
10. List different types of stabilizers and use of a stabilizer.

## PART—B


10×5=50

- Instructions :** (1) Answer *any five* questions.  
 (2) Each question carries **ten** marks.  
 (3) Answers should be comprehensive and the criterion for valuation is the content but not the length of the answer.

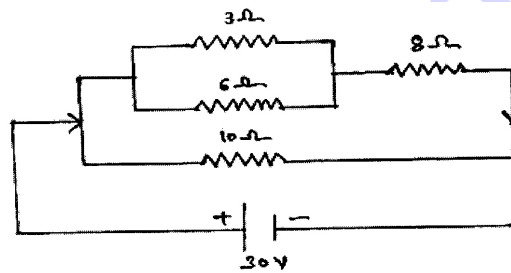
11. (a) Explain the laws of resistance. 4  
 (b) In the circuit given below, calculate the current in each resistor and total current : 6



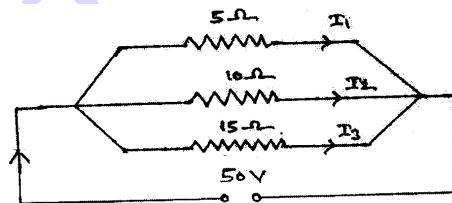12. (a) Derive an equation for equivalent resistance when two resistors connected in parallel. 5  
 (b) Find the current in each resistance of the circuit given below : 5



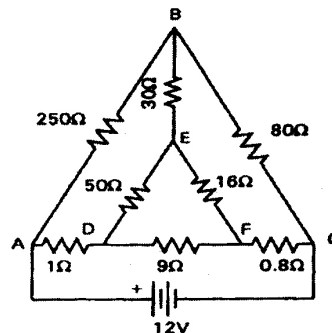13. Determine the current through 30Ω resistor by applying star-delta transformation in the following circuit :



- \* 14. (a) State the limitations of Ohm's law. 4  
 (b) Define the terms (i) instantaneous value, (ii) maximum value and (iii) RMS value. 6
15. (a) State and explain Faraday's law of electromagnetic induction. 6  
 (b) An  $R$ - $L$ - $C$  series circuit with resistance 1 ohm, inductance 0.1 mH and capacitance 100 F is supplied with 220 volts. Calculate the resonant frequency. 4
16. (a) List the difference between rheostat and potentiometer. 4  
 (b) Explain how resistor value can be determined based on colour codes. Find the colour code for resistance of 0.1 1%. 6
17. Draw and explain the input and output characteristics of transistor in CE configuration. 10
18. (a) Explain the working principle of UPS with block diagram. 4  
 (b) Explain the formation of  $P$ - $N$  junction diode. 6

\*\*\*