

4232

BOARD DIPLOMA EXAMINATION, (C-14)

MARCH /APRIL-2019

DCME - THIRD SEMESTER EXAMINATION

BASIC ELECTRICAL &amp; ELECTRONICS ENGINEERING

Time: 3 Hours]

[Max.Marks:80M

**PART-A****3x10=30M**

**Instructions:** 1) Answer **all** questions. Each question carries **three** marks.  
2) Answer should be brief and straight to the point and shall not exceed five simple sentences.

- 1) State Ohm's law.
- 2) Find the specific resistance of 60 cm length copper wire whose resistance is  $0.1 \Omega$  having a diameter 0.2 mm.
- 3) Differentiate between active and passive circuits.
- 4) Three resistances of 6 , 4 and 3 are connected in delta connection. Find their equivalent star values.
- 5) State Fleming's right hand rule.
- 6) List the resistors on the basis of materials for their construction.
- 7) Distinguish between conductor, semi-conductor and insulator on the basis of valance electron.
- 8) List the applications of semiconductor diodes.
- 9) Draw the I.S.I symbols of PNP and NPN Transistors.
- 10) List different types of stabilizer?

## PART-B

5x10=50M

**Instructions:** 1) Answer any **five** questions. Each question carries **ten** marks.  
2) The answers should be comprehensive and the criteria for valuation is the content but not the length of answer.

- 11) (a) Derive the Expression for Resistances in parallel (Two Resistances)  
(b) Three Resistances 15  $\Omega$ , 10  $\Omega$  and 8  $\Omega$  are connected in parallel across a supply voltage of 120 V. Find (i) The Resistance (ii) The current through each resistor (iii) The voltage in 8  $\Omega$  resistance. (5+5)
- 12) (a) Develop the formula for resistance at any temperature  $R_t = R_o(1 + \alpha_o t)$   
(b) The resistance of copper coil at 15°C is 25  $\Omega$  and at 75°C is 30  $\Omega$ . Find the Temperature Coefficient of Resistance at 0°C (5+5)
- 13) (a) State Kirchhoff's current law, and Voltage law.  
(b) Three resistances  $R_1$ ,  $R_2$  and  $R_3$  are connected in Delta. Derive their equivalent star resistances. (5+5)
- 14) (a) Explain the concept of self and mutual inductances.  
(b) State (i) Lenz's law (ii) Fleming's left hand rule. (5+5)
- 15) (a) Distinguish between Potentiometer and Rheostat and write their uses.  
(b) State PTC and NTC resistors and write their applications. (5+5)
- 16) (a) Write any five differences between P-type N-type semiconductors.  
(b) Describe the operation of PN junction with forward bias. (5+5)
- 17) (a) Explain junction, branch and loop in circuits.  
(b) State Co-efficient of coupling. (6+4)
- 18) (a) Describe the atomic structure of Germanium, silicon semi-conductor materials.  
(b) Write brief notes on Maintenance Free batteries. (6+4)

\* \* \*