



C14-CM-303/C14-IT-303

4233

**BOARD DIPLOMA EXAMINATION, (C-14)**  
**OCT/NOV—2015**  
**DCME—THIRD SEMESTER EXAMINATION**  
**DIGITAL ELECTRONICS**

Time : 3 hours ]

[ Total Marks : 80

---

**PART—A**

3×10=30

**Instructions :** (1) Answer **all** questions.

(2) Each question carries **three** marks.

(3) Answers should be brief and straight to the point and shall not exceed *five* simple sentences.

1. Draw the symbols of NAND and AND gates along with truth table. 1½+1½=3
2. Draw the diagram of full adder. 3
3. Draw 4-bit parallel adder diagram using full adder. 3
4. Draw the symbol of D flip-flop along with truth table. 1½+1½=3
5. Define propagation delay and power dissipation of logic family. 1½+1½=3
6. Draw the NAND latch with truth table. 1½+1½=3
7. Draw the diagram of 4-bit ring counter. 3
8. State the need for a register. 3

- \* 9. Differentiate between static RAM and dynamic RAM. 1×3=3
10. List the applications of demultiplexer. 1×3=3

**PART—B**

10×5=50

**Instructions :** (1) Answer *any five* questions.  
 (2) Each question carries **ten** marks.  
 (3) Answers should be comprehensive and the criterion for valuation is the content but not the length of the answer.

11. (a) Explain the working of EX-OR gate with truth table. 5  
 (b) Simplify the following Boolean expression :  

$$AB + A(B + C) + B(B + C)$$
 5
12. Draw and explain the working of 4-bit 2's complement adder and subtractor. 5+5
13. Draw and explain the clocked R-S flip-flop. 4+6
14. Draw and explain the operation of T flip-flop. 4+6
15. Draw and explain the operation of UP-DOWN counter. 4+6
16. Explain the working of universal shift register (74194). 10
17. Explain the data movement in the following registers : 5+5  
 (a) Serial-in-Parallel-out  
 (b) Parallel-in-Serial-out
18. (a) Explain the 4 to 1 multiplexer with diagram. 5  
 (b) Write any five applications of counter. 5

\*\*\*