



C14-CM-303/C14-IT-303

4233

**BOARD DIPLOMA EXAMINATION, (C-14)**  
**MARCH/APRIL—2018**  
**DCME—THIRD SEMESTER EXAMINATION**

DIGITAL ELECTRONICS

Time : 3 hours ]

[ Total Marks : 80

---

**PART—A**

3×10=30

**Instructions :** (1) Answer **all** questions.

(2) Each question carries **three** marks.

(3) Answers should be brief and straight to the point and shall not exceed *five* simple sentences.

1. Draw the symbols and truth tables of basic gates. 1+1+1
2. State De Morgan's laws. 1½+1½
3. Draw and explain the logic circuit of a half-adder. 1+1+1
4. Explain the levels of integration. 3
5. Define the terms (a) compatibility and (b) fan-out. 1½+1½
6. Define the terms (a) preset input and (b) clear input. 1½+1½
7. List the applications of counters. 3

- \* 8. Distinguish between ROM and RAM. 3
9. Define a register. 3
10. Define the terms (a) multiplexer and (b) encoder.  $1\frac{1}{2}+1\frac{1}{2}$

**PART—B**

10×5=50

**Instructions :** (1) Answer *any five* questions.

(2) Each question carries **ten** marks.

(3) Answers should be comprehensive and the criterion for valuation is the content but not the length of the answer.

11. Explain the working of 4-bit parallel adder with the help of suitable circuit and example. 5+5
12. Reduce the following function using K-map technique : 10  
 $F(A, B, C, D) \quad m(1, 3, 4, 5, 7, 9, 11, 13, 15)$
13. Draw and explain the working of *R-S* flip-flop using NAND gates. 3+3+4
14. With a neat sketch, explain the working of edge triggered *J-K* flip-flop. 3+3+4
15. Draw the diagram of Mod-16 synchronous counter and explain the operation with the help of timing diagram. 3+3+4
16. (a) List the drawbacks of ripple counter. 5  
 (b) Draw the circuit diagram of multiplexer and explain the operation. 2+3
17. Draw and explain the working of shift right register. 4+6
- \* 18. Draw and explain the operation of IC 74194 universal shift register. 4+6

\*\*\*