



C14-CM-303/IT-303

4233

BOARD DIPLOMA EXAMINATION, (C-14)  
OCT/NOV—2018  
DCME—THIRD SEMESTER EXAMINATION  
DIGITAL ELECTRONICS

Time : 3 hours ]

[ Total Marks : 80

---

PART—A

3×10=30

**Instructions** : (1) Answer **all** questions.  
(2) Each question carries **three** marks.  
(3) Answers should be brief and straight to the point and shall not exceed *five* simple sentences.

1. State De Morgan's Laws.
2. What is the importance of K-Map?
3. Differentiate between serial adder with parallel adder.
4. Define positive and negative logic levels.
5. Differentiate Synchronous and Asynchronous inputs of a flip flop.
6. What is meant by racing in JK flip flop? How it can be eliminated?

- \* 7. List the any three applications of counters.
- 8. State the need for a Register.
- 9. Write the differences between ROM and RAM.
- 10. List any three applications of Demultiplexers.

**PART—B**

10×5=50

**Instructions** : (1) Answer *any five* questions.

(2) Each question carries **ten** marks.

(3) The answers should be comprehensive and the criterion for valuation is the content but not the length of the answer.

- 11. Explain Realization of AND, OR, NOT, EX-OR gates using NAND gate only and NOR gate only.
- 12. Explain the working of 4-Bit parallel adder with neat diagram.
- 13. Draw and explain the working of Clocked RS Flip Flop.
- 14. Explain the operation of T Flip Flop with diagram, truth table and waveforms.
- 15. Explain the working of Decade counter with neat diagram.
- 16. (a) Draw and explain the operation of a 4-bit ring counter.  
(b) Explain the operation of a 4×1 Multiplexer with neat diagram.
- \* 17. Draw and explain the working of 4-bit Shift Left and Shift Right Registers.
- 18. What is meant by data transfer in registers? Explain any two types of data transfer?

\*\*\*