

*
4233

BOARD DIPLOMA EXAMINATION, (C-14)

MARCH /APRIL-2019

DCME - THIRD SEMESTER EXAMINATION

DIGITAL ELECTRONICS

Time: 3 Hours]

[Max.Marks: 80M

PART-A

3x10=30M

Instructions: 1) Answer **all** questions. Each question carries **three** marks.
2) Answer should be brief and straight to the point and shall not exceed five simple sentences.

- 1) Write any three postulates of Boolean algebra.
 - 2) Draw logic circuit of half adder with its truth table.
 - 3) Write the differences between parallel adder and serial adder.
 - 4) Write the Classification of different Logic Families?
 - 5) State the need for JK Master Slave Flip Flop.
 - 6) Draw clocked RS Flip Flop with its truth table.
 - 7) Distinguish between Asynchronous and Synchronous counters.
 - 8) Define a Register and state the need of it.
 - 9) Differentiate between static RAM and dynamic RAM.
 - 10) List any three applications of Demultiplexers.
- *
*

PART-B

5x10=50M

Instructions: 1) Answer any **five** questions. Each question carries **ten** marks.
2) The answers should be comprehensive and the criteria for valuation is the content but not the length of answer.

- 11) a) Explain EX-OR and EX-NOR gates 3
b) Explain Realization of AND, OR, NOT gates using NAND gate only. 5
c) Explain why NAND and NOR are called Universal gates. 2
- 12) a) Simplify the following expression using K-Map
 $Y = \sum m(0,1,2,3,5,7,8,9,10,11,13,14,15)$ 5
b) Explain working of 2's complement Adder Subtractor with neat diagram. 5
- 13) Draw and explain the working of D Flip-Flop with truth table and timing diagram.
- 14) Draw and explain the working of JK Master Slave Flip Flop.
- 15) Draw and explain the operation of a programmable counter.
- 16) a) Explain briefly the working of DOWN counter with neat diagram. 5
b) Draw and explain the operation of 10 X 4 encoder. 5
- 17) Explain the data transfer in the following registers with neat diagram.
a) Serial in - Serial out b) Serial in - Parallel out (5+5)
- 18) Explain the use of shift register as memory with neat diagram. 10

* * *