

\*



C20-CM-302

**7235**

**BOARD DIPLOMA EXAMINATION, (C-20)**

**FEBRUARY/MARCH — 2022**

**DCME - THIRD SEMESTER EXAMINATION**

**DIGITAL ELECTRONICS**

*Time : 3 hours ]*

*[ Total Marks : 80*

**PART—A**

3×10=30

- Instructions :** (1) Answer **all** questions.  
(2) Each question carries **three** marks.  
(3) Answers should be brief and straight to the point and shall not exceed five simple sentences.

1. Convert  $12.5_{(10)}$  into binary.
2. Give the table showing octal digits from 0 to 7 and binary values.
3. Define logic gate.
4. Construct OR gate from NOR gate.
5. Define flip-flop.
6. What is the need for master slave flip-flop?
7. Define a counter.
8. Define register.
9. State the importance of data selector.
10. List the applications of multiplexers.

\*

**PART—B**

8×5=40

- Instructions :** (1) Answer **all** questions.  
 (2) Each question carries **eight** marks.  
 (3) Answers should be comprehensive and criterion for valuation is the content but not the length of the answer.

- 11.** (a) What is the value of (i)  $10110011_{(2)}$  into decimal and (ii)  $10101100_{(2)}$  into hexadecimal.

**(OR)**

- (b) Give the steps in forming 8421 code and 2421 code for the values from 0 to 9, comment on how these two codes are different.

- 12.** (a) Give the steps of how the Products of Sum (POS) method gives the Boolean expression of the below truth table :

A	B	C	Y
0	0	0	0
1	0	0	1
0	1	0	1
1	0	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

**(OR)**

- (b) Give the steps of how the K-map reduces the given expression  $Y = \Sigma m(3,5,6,8,10,11,14)$ .

\*

13. (a) Give the reasons for supporting the statement RST flip-flop is more suitable than RS flip-flop with truth table.

**(OR)**

- (b) Give reasons why flip-flop is more suitable than NAND latch with diagrams.

14. (a) Give the steps to modify the synchronous counter as mod-10 counter with waveforms and truth table.

**(OR)**

- (b) Draw the circuit diagram of a register that takes data in serial and takes out data in serial with working principle and steps for processing the data.

15. (a) Suggest the name of a decoder for transmitting 10 outputs with the 4line controllers with proper explanation.

**(OR)**

- (b) Recommend a multiplexer using which 8 inputs are transmitted on a line with proper explanation.

**PART—C**

10×1=10

**Instructions :** (1) Answer the following question.

(2) The question carries **ten** marks.

(3) Answer should be comprehensive and criterion for valuation is the content but not the length of the answer.

16. Construct a 4-bit adder for adding two numbers at a time, by using two half adders for adding bits at each column of two numbers.

★ ★ ★