



C09-EC-303

3235

**BOARD DIPLOMA EXAMINATION, (C-09)
MARCH/APRIL—2014
DECE—THIRD SEMESTER EXAMINATION
ELECTRONIC CIRCUITS—I**

Time : 3 hours]

[Total Marks : 80

PART—A

3×10=30

Instructions : (1) Answer **all** questions.
(2) Each question carries **three** marks.
(3) Answers should be brief and straight to the point and shall not exceed *five* simple sentences.

1. State the need for DC power supply for electronic circuits.
2. Compare between half-wave and centre tapped full-wave rectifiers.
3. List the advantages of IC regulators.
4. Why is CE mode commonly used in amplifier circuits?
5. Define h-parameters of a transistor.
6. Explain the need for stabilization.
7. Mention the advantages of FET over BJT.
8. Mention the applications of varactor diode.

- * 9. Classify the ICs.
10. Define (a) CMRR, (b) input offset voltage and (c) input offset current.

PART—B

10×5=50

Instructions : (1) Answer *any five* questions.
 (2) Each question carries **ten** marks.
 (3) Answers should be comprehensive and the criterion for valuation is the content but not the length of the answer.

11. (a) Describe the working of CLC filter. 5
 (b) Explain the operation of online UPS with the help of diagram. 5
12. Draw the diagram of bridge rectifier and explain its working with waveforms. 10
13. Draw the circuit of self-bias and explain how it provides stabilization and derive the expression for stability factor. 10
14. Draw the circuit of two-stage transformer coupled amplifier and explain its working and draw its frequency response. 10
15. Draw the circuit of n-channel FET and explain its working and draw its drain characteristics. 10
16. (a) What are the differences between JFET and MOSFET? 5
 (b) List any five applications of UJT. 5
17. (a) Compare between discrete and integrated circuits. 5
 (b) Explain the fabrication of resistors. 5
- * 18. (a) Explain how op-amps work as inverting amplifier. 5
 (b) Mention any five ideal op-amps characteristics. 5
