



C09-EC-305

3237

**BOARD DIPLOMA EXAMINATION, (C-09)
OCT/NOV—2013
DECE—THIRD SEMESTER EXAMINATION
DIGITAL ELECTRONICS**

Time : 3 hours]

[Total Marks : 80

PART—A

Instructions : (1) Answer **all** questions.

(2) Each question carries **three** marks.

(3) Answer should be brief and straight to the point and shall not exceed *five* simple sentences.

1. Explain the uses of the following alphanumeric codes :

(a) ASCII

(b) EBCDIC

2. Construct a given decimal number into octal and hexadecimal number system :

(a) 908

(b) 76

(c) 753

3. State De Morgan's theorems.

*

C09-EC-305

4. State the need for a tri-state buffer.
5. Draw the logic circuit of one bit comparator.
6. Write the need for preset and clear inputs.
7. List any two IC numbers for—
 - (a) flip-flops;
 - (b) registers;
 - (c) counters.
8. Draw NAND and NOR latches.
9. Define the following terms :
 - (a) Resolution
 - (b) Monotonicity
 - (c) Accuracy
10. Write any three differences between flash ROM and NV RAM.

PART—B

Instructions : (1) Answer *any five* questions.

(2) Each question carries **ten** marks.

(3) Answers should be comprehensive and the criterion for valuation is the content but not the length of the answer.

11. Draw and explain CMOS NAND gate and explain its operation. 4+6

* /3237

2

[Contd...

*

*

12. By applying De Morgan's theorems and postulates simplify the logic expressions :

(a) $\overline{(A \ B) \overline{CD} \ E \ \overline{F}}$ 5

(b) $\overline{\overline{(A \ B)} \ \overline{C}}$ 5

13. Draw and explain 2's complement parallel adder-subtractor. 4+6

14. (a) Draw and explain master/slave J-K flip-flop. 5

(b) Draw and explain level clocked D flip-flop with the help of truth table. 5

15. (a) Realise a half-adder using NOR gates only. 4

(b) Draw and explain 3 8 decoder. 3+3

16. Draw and explain the working of universal shift register. 4+6

17. Explain A-D conversion using successive approximation method. 4+6

18. (a) Explain the working principle of NV RAM. 3+3

(b) Differentiate between EEPROM and UVPROM. 4

*
