



C09-EC-305

3237

**BOARD DIPLOMA EXAMINATION, (C-09)
MARCH/APRIL—2017
DECE—THIRD SEMESTER EXAMINATION**

DIGITAL ELECTRONICS

Time : 3 hours]

[Total Marks : 80

PART—A

3×10=30

Instructions : (1) Answer **all** questions.

(2) Each question carries **three** marks.

(3) Answers should be brief and straight to the point and shall not exceed *five* simple sentences.

1. Convert the following binary numbers into decimal numbers :

(a) 1101_2

(b) $1011\ 11_2$

(c) 1111_2

2. Express the decimal 5280 in Excess-3 code.

3. List three digital logic families.

4. Realize half-adder circuit using NAND gates only.

5. State the need for a tri-state buffer.

6. List the types of register.

- * 7. Draw a level clocked T flip-flop.
8. What is the need of preset and clear inputs in flip-flops?
9. Define the terms resolution and accuracy of D/A converter.
10. Compare static RAM with dynamic RAM.

PART—B

10×5=50

Instructions : (1) Answer *any five* questions.
 (2) Each question carries **ten** marks.
 (3) Answers should be comprehensive and the criterion for valuation is the content but not the length of the answer.

11. (a) State any five Boolean postulates. 5
 (b) Draw the logic circuits for the realization of AND, OR and NOT operations using NOR gates only. 5
12. (a) Write Boolean expression of product of maxterms from the following truth table : 5

Inputs			Output
A	B	C	X
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

- (b) Use Karnaugh map to simplify the following Boolean expression : 5

$$Y = \overline{A}\overline{B} + \overline{A}B + AB$$

- * **13.** Draw and explain the logic circuit of 4 to 1 multiplexer.
- 14.** Draw a 2's complement parallel adder/subtractor circuit and explain its working.
- 15.** Draw and explain the working of ring counter.
- 16.** (a) Draw and explain the operation of NOR latch. 5
(b) What is the necessity of clock in flip-flop? List the types of triggering. 5
- 17.** (a) Write a short note on memory modules used in computers. 5
(b) Distinguish between EEPROM and UMPROM. 5
- 18.** Explain D/A conversion using R-2R ladder network with a circuit diagram.
