



C14-EC-305

4241

**BOARD DIPLOMA EXAMINATION, (C-14)
OCT/NOV—2018
DECE—THIRD SEMESTER EXAMINATION**

DIGITAL ELECTRONICS

Time : 3 hours]

[Total Marks : 80

PART—A

3×10=30

Instructions : (1) Answer **all** questions.
(2) Each question carries **three** marks.
(3) Answers should be brief and straight to the point and shall not exceed *five* simple sentences.

1. Draw the basic logic gates AND, OR, NOT Gates with Truth tables.
2. Convert $(1101.101)_2$ into octal, hexa-decimal and decimal numbers.
3. State the need for a tristate buffer.
4. Write the importance of Parity bit.
5. List the important characteristics of Digital ICS.
6. State the need for a register.
7. Draw Half adder circuit with truth table.
8. Draw NAND Latch with Truth Table.
9. List any three applications of flip flops.
10. Distinguish between RAM and ROM.

PART-B

10×5=50

- * **Instructions :** (1) Answer *any five* questions.
(2) Each questions carries **ten** marks.
(3) Answers should be comprehensive and the criteria for valuation are the content but not the length of the answer.

11. Simplify the Boolean expression using k map and implement using basic Gates

$$F(A,B,C,D) = A'B'D'+ABC'D'+A'BD+ABCD'$$

- 12.** Draw and explain TTL NAND Gate with Totem pole output.
- 13.** State and explain De-Morgan's theorems.
- 14.** Draw and explain 2's compliment parallel adder/subtractor circuit.
- 15.** a) Draw and explain the operation of 4×1 multiplexer.
b) List applications of multiplexer.
- 16.** Draw and explain clocked SR flip flop using NAND Gates with truth table.
- 17.** Explain the working of 4 bit shift left register with a circuit and timing diagram.
- 18.** Draw and explain the working of 4 bit asynchronous counter.

* * *