

*



C14-EC-306

4242

BOARD DIPLOMA EXAMINATION, (C-14)
MARCH/APRIL—2021
DECE - THIRD SEMESTER EXAMINATION
ELECTRICAL TECHNOLOGY

Time : 3 hours]

[Total Marks : 80

PART—A

4×5=20

- Instructions :** (1) Answer *any five* questions.
(2) Each question carries **four** marks.
(3) Answers should be brief and straight to the point and should *not* exceed five simple sentences.

1. State the condition for resonance in RLC Circuits.
2. A pure inductance coil having an inductance of 8H is connected in series with a capacitor of 50 μ F capacitance across 230 V 50 Hz. Find the net reactance.
3. State Faraday's laws of electromagnetic induction.
4. What is need for a Starter?
5. Define a power plant.
6. Write the e.m.f. equation of a Transformer.
7. What are the different losses of a Transformer?

*

8. Define coefficient of coupling.
9. Define synchronous speed of an Induction Motor.
10. What are the applications of Servo Motor?

PART—B

15×4=60

Instructions : (1) Answer *any four* questions.
(2) Each question carries **fifteen** marks.
(3) Answers should be comprehensive and criteria for valuation is the content but *not* the length of the answer.

11. The two given vectors are $Z_1 = 5 - j2$ and $Z_2 = 3 - j8$. Find $Z_1 + Z_2$ and $Z_1 - Z_2$.
12. In a series RLC circuit having resistance of 12Ω , inductance 0.15 H and capacitance of $100\ \mu\text{F}$ with a 100 V 50 Hz supply. Calculate the value of impedance current, power factor and power consumed.
13. Explain the dynamically and statically induced EMF.
14. Explain the characteristics of DC Shut motor.
15. A symmetrical 3ϕ 400 V system supplied a balanced delta connected load, the current in each branch circuit is 30 A and phase angle is 30° lag. Find (i) The line current and (ii) The total power consumed.
16. Explain the construction and working of Auto Transformer.
17. With a neat waveform and vector diagram explain the principle of production of rotating magnetic field in 3ϕ induction machines.
18. Explain the working of an Alternator.

*

★ ★ ★