



C14-EC-403

4457

BOARD DIPLOMA EXAMINATION, (C-14)
OCT/NOV—2018
DECE—FOURTH SEMESTER EXAMINATION
NETWORK ANALYSIS

Time : 3 hours]


[Total Marks : 80

PART—A

3×10=30

- Instructions :** (1) Answer **all** questions.
(2) Each question carries **three** marks.
(3) Answers should be brief and straight to the point

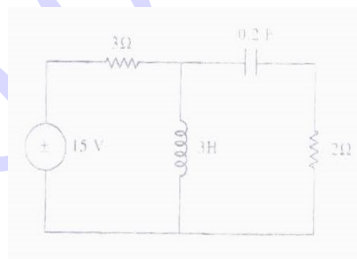1. Define ideal voltage source and practical voltage source.
2. Define dot rule in coupled circuits.
3. Define node, loop and branch of a network.
4. Draw the dual of given network



5. Define superposition theorem.
6. Define maximum power transfer theorem for AC load.
7. Define initial condition and steady state response in transients.

8. Define the Y-parameters of a two-port network.

*

9. Define the terms Neper and Decible.


10. Distinguish between attenuators and equalizers.

PART-B

10×5=50

- Instructions :** (1) Answer *any five* questions.
 (2) Each questions carries **ten** marks.
 (3) Answers should be comprehensive.

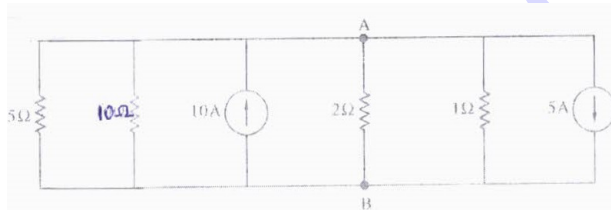
11. (a) State Kirchhoff's current law and Kinchhoff's voltage law.
 (b) Find the voltages on 10Ω resistor using KCL.



12. Find the currents I_A , I_B , I_C using mesh analysis.




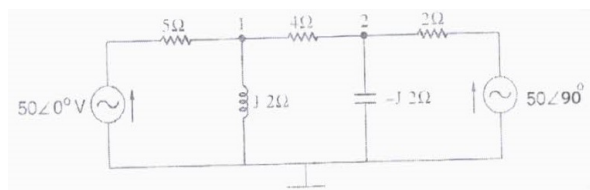13. Determine voltages at nodes 1 and 2 for the circuit given below.




14. Verify reciprocity theorem to find the voltage V_x


*

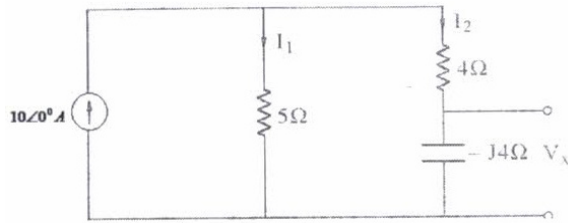

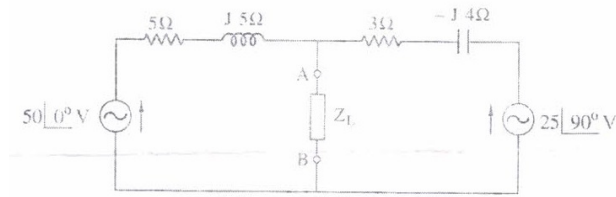
15. Determine load impedance Z_L for maximum power transfer and find the maximum power.



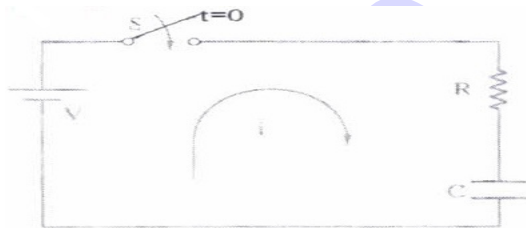16. Derive the expressions for Voltages across R and C for for $t > 0$, When switch is closed at $t=0$.



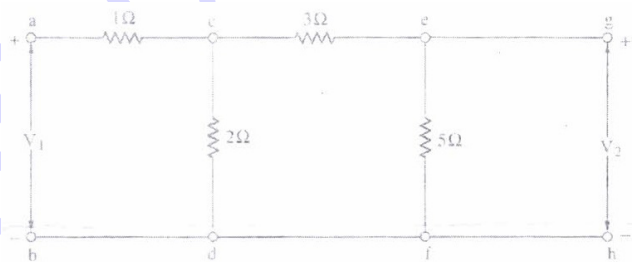17. Find the Z parameters for the two port network given below.



18. Derive the expression for characteristic impedance of a symmetrical Π -Network.

*