



C16-EC-302

6233

BOARD DIPLOMA EXAMINATION, (C-16)
MARCH/APRIL—2018
DECE—THIRD SEMESTER EXAMINATION
ELECTRONIC CIRCUITS

Time : 3 hours]

[Total Marks : 80

PART—A

3×10=30

Instructions : (1) Answer **all** questions.
(2) Each question carries **three** marks.
(3) Answers should be brief and straight to the point and shall not exceed *five* simple sentences.

1. Explain the thermal runaway.
2. Write the importance of heat sink.
3. Draw the circuit diagram of two-stage RC-coupled amplifier.
4. Explain the concept of positive feedback.
5. Compare the characteristics of the negative feedback amplifiers.
6. List the applications of class C amplifier.
7. Explain the Barkhausen criteria in oscillators.
8. List different linear wave-shaping networks.

- * 9. Draw the circuit diagram of shunt diode positive clipper.
10. Explain the photovoltaic effect.

PART—B

10×5=50

Instructions : (1) Answer *any five* questions.

(2) Each question carries **ten** marks.

(3) Answers should be comprehensive and the criterion for valuation is the content but not the length of the answer.

11. Explain diode compensation technique with a neat circuit diagram. 3+7
12. (a) Define stability factors and give their equations. 6
(b) Explain the importance of bias stabilization. 4
13. Explain the operation of transformer-coupled amplifier and draw the frequency response. 7+3
14. (a) Derive the expression for the gain of negative feedback amplifier. 4
(b) Draw the block diagram of current series and voltage shunt feedback amplifiers. 6
15. Explain the working of class AB push-pull amplifier circuit. 10
16. Explain the working of Colpitts oscillator with a neat circuit diagram. 10
17. Explain the working of Schmitt trigger circuit with waveform.
18. (a) Explain the operation of transistor series voltage regulator. 7
(b) Explain the disadvantage of series voltage regulator. 3
