



C09-EE-303

3241

BOARD DIPLOMA EXAMINATION, (C-09)
MARCH/APRIL—2017
DEEE—THIRD SEMESTER EXAMINATION
ELECTRICAL CIRCUITS

Time : 3 hours]

[Total Marks : 80

PART—A

3×10=30

Instructions : (1) Answer **all** questions.

(2) Each question carries **three** marks.

(3) Answer should be brief and straight to the point and shall not exceed *five* simple sentences.

1. Define active circuit and passive circuit.
2. State Thevenin's theorem.
3. Define average value, form factor and peak factor.
4. Derive the RMS value of a full-wave rectified sine waveform.
5. Perform and represent in polar form (a) $A = 5 - j6$ and $B = 6 + j8$, where $A = 5 - j6$ and $B = 6 + j8$.
6. Derive an expression for current in pure capacitive circuit, when an alternating voltage $v = V_m \sin t$ is applied.
7. State the formula for power factor in $R-L-C$ series circuit.
8. Compare series with parallel resonant circuits.

- * 9. Give the advantage of polyphase system.
10. List the relation between line values and phase values in star and delta connected systems.

PART—B

10×5=50

Instructions : (1) Answer *any five* questions.

(2) Each question carries **ten** marks.

(3) Answers should be comprehensive and the criterion for valuation is the content but not the length of the answer.

11. (a) State Kirchoff's laws. 4
- (b) Determine the equivalent resistance across *AB* of the circuit shown in Fig. 1 : 6

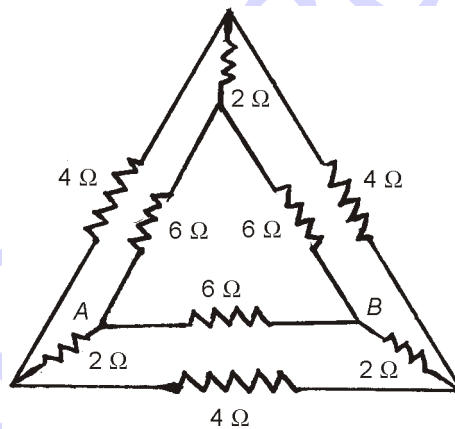


Fig. 1

12. Find the current through 20 Ω resistance of the network (Fig. 2) by using superposition theorem : 10

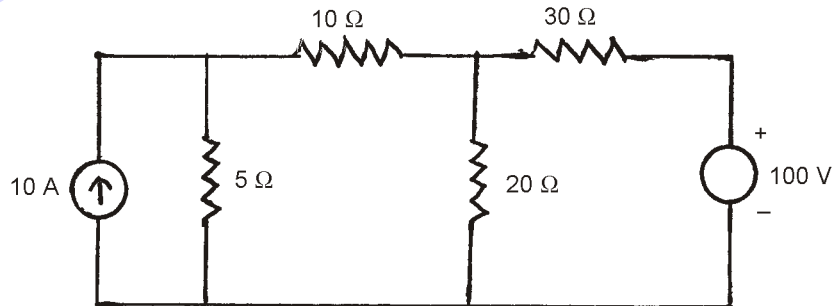


Fig. 2

- * 13. (a) State and explain the maximum power transfer theorem. 7
- (b) The equation of an alternating current is $i = 100 \sin 628t$. Determine—
- (i) RMS value;
- (ii) average value;
- (iii) time period. 3
14. (a) Convert the following rectangular to polar or polar to rectangular :
- (i) $4 - j6$
- (ii) $20 \angle 30^\circ$
- (b) Show the average power consumed in an inductor and a capacitor is zero. 6
15. A resistance of 10Ω and inductance of 0.1 H are connected in series across a supply of 220 V and 50 Hz . Determine (i) the impedance, (ii) current flowing, (iii) power factor, (iv) the phase angle between V and I and (v) total power consumed. 10
16. Two impedances $Z_1 = 10 - j15 \Omega$ and $Z_2 = 6 + j8 \Omega$ are connected in parallel. If the total current supplied is 15 A , find the voltage applied, current and the power taken by each branch. 10
17. A series RLC circuit consists of 1000Ω , $L = 100 \text{ mH}$ and $C = 10 \text{ pF}$. If the applied voltage across the circuit is 100 V , find (a) resonant frequency, (b) current at resonance and (c) Q -factor of the circuit. 10
18. A balance 3- star connected load of 150 kW takes a leading current of 100 A with a line voltage of 1100 V at 50 Hz . Find the power factor and circuit constants and draw its vector diagram. 10
