



C09-EE-306

3244

BOARD DIPLOMA EXAMINATION, (C-09)

OCT/NOV—2014

DEEE—THIRD SEMESTER EXAMINATION

ELECTRONICS ENGINEERING

Time : 3 hours]

[*Total Marks* : 80

PART—A

3×10=30

Instructions : (1) Answer **all** questions.

(2) Each question carries **three** marks.

(3) Answer should be brief and straight to the point and shall not exceed *five* simple sentences.

1. Draw the circuit diagram of a half-wave rectifier. 3
2. State the need for filter in power supply circuits. 3
3. (a) Draw the input and output waveform of centre tapped full-wave rectifier. 1½
(b) Draw the equivalent circuit of UJT. 1½
4. Draw the symbols of (a) *n*-channel FET, (b) LED and (c) photo-diode. 3
5. List any three applications of LED. 3
6. Draw collector-to-base bias circuit. 3
7. Classify amplifiers based on frequency and coupling. 3
8. Draw the circuit diagram of class-A power amplifier. 3

- * 9. State the Barkhausen's conditions for sustained oscillations. 3
- 10. List the applications of CRO. 3

PART—B

10×5=50

Instructions : (1) Answer *any five* questions.

(2) Each question carries **ten** marks.

(3) Answers should be comprehensive and the criterion for valuation is the content but not the length of the answer.

- 11. Explain the working principle of bridge rectifier with waveforms. 10
- 12. Explain the construction and working principle of JFET. 4+6
- 13. (a) Explain the potential divider biasing (self-bias) method. 6
- (b) List the causes for instability of biasing in a transistor. 4
- 14. Explain the operation of two-stage RC coupled amplifier. Draw its frequency response. 8+2
- 15. (a) List the advantages of negative feedback in amplifiers. 5
- (b) Compare voltage and power amplifiers. 5
- 16. Explain the operation of operational amplifier as (a) summer and (b) integrator. 5+5
- 17. Explain the working principle of Colpitts oscillator. 10
- * 18. Draw and explain the internal block diagram of 555 timer IC. 4+6
