



C09-EE-402

3474

BOARD DIPLOMA EXAMINATION, (C-09)

OCT/NOV—2013

DEEE—FOURTH SEMESTER EXAMINATION

AC MACHINES—I

Time : 3 hours ]

[ Total Marks : 80

---

**PART—A**

**Instructions** : (1) Answer **all** questions.

(2) Each question carries **three** marks.

(3) Answer should be brief and straight to the point and shall not exceed *five* simple sentences.

1. Briefly explain the equivalent circuit parameters obtained from OC and SC test of a transformer.
2. Classify the transformers basing on number of phases and construction.
3. List the various losses in a transformer and explain how the copper loss varies with load current.
4. Write any three advantages of welding transformer.
5. Draw the connection diagram of delta-star configuration of 3-phase transformer.

\*

6. Draw the circuit diagram for measurement of power in 1-phase circuit with the help of instrument transformers.
7. What are the advantages of distributed winding?
8. Draw the phasor diagram of an alternator for a lagging power factor load.
9. Explain the effect of armature reaction of alternator for zero power factor leading load.
10. State the conditions for synchronization of an alternator.

**PART—B**

**Instructions :** (1) Answer *any five* questions.

(2) Each question carries **ten** marks.

(3) Answers should be comprehensive and the criterion for valuation is the content but not the length of the answer.

11. Two single-phase transformers with an equal voltage ratio are running in parallel and supplying a load of 100 kW at 0.8 pf lag. The equivalent impedances of the transformers as referred to secondary are  $(0.5 + j3)$  and  $(0.6 + j10)$  . Find the load shared by each transformer. 5+5

12. (a) Derive an EMF equation of single-phase transformer. 5  
(b) The EMF per turn of a 260/117 V, 1 kVA single-phase power transformer is approximately 13 volts. Calculate—
  - (i) the number of primary and secondary turns; 3
  - (ii) the net cross-sectional area of the core, for a maximum flux density of the core of 1.4 tesla. 2

\*

- 13.** A transformer has a maximum efficiency of 98% at 15 kVA at UPF. During the day, it is loaded as follows :
- 10 hours—3 kW at 0.6 pf
  - 5 hours—10 kW at 0.8 pf
  - 5 hours—18 kW at 0.9 pf
  - 4 hours—No-load
- Calculate the all-day efficiency of a transformer. 10
- 14.** (a) Develop the exact equivalent circuit of a 1-phase transformer. 5
- (b) Develop the vector diagram for a transformer on load for leading power factor. 5
- 15.** (a) Briefly explain the necessity of transformer cooling . 5
- (b) List any five applications of auto-transformer. 5
- 16.** (a) Explain the procedure for conducting open circuit test on an alternator with a neat sketch. 5
- (b) Differentiate between the salient pole type rotor in any five aspects w.r.t. non-salient pole type rotor. 5
- 17.** (a) For a 3-phase winding with 4-slots per pole per phase and with the coil span of 10 slots, evaluate the distribution and pitch factor. 5
- (b) Explain the working principle of an alternator. 5
- 18.** Two AC generators running in parallel supply lighting load of 2000 kW and a motor load of 4000 kW at a PF of 0.8 lagging. One machine is loaded to 2400 kW at 0.95 PF lagging. What is the kW output and PF of the second machine? 10

\*\*\*