



C14-EE-303

4245

BOARD DIPLOMA EXAMINATION, (C-14)
OCT/NOV—2015
DEEE—THIRD SEMESTER EXAMINATION
ELECTRICAL CIRCUITS

Time : 3 hours]

[Total Marks : 80

PART—A

3×10=30

- Instructions :** (1) Answer **all** questions.
(2) Each question carries **three** marks.
(3) Answer should be brief and straight to the point and shall not exceed *five* simple sentences.

1. Define active and passive circuits. 1½+1½=3
2. State Kirchhoff's laws. 1½+1½=3
3. Define the following terms : 1+1+1=3
 - (a) Cycle
 - (b) Time period
 - (c) Amplitude
4. Define phase and phase difference of an alternating quantity. 1½+1½=3
5. Convert the following rectangular to polar or polar to rectangular : 1½+1½=3
 - (a) $3 - j6$
 - (b) $100\angle 45^\circ$

- * 6. Derive the relation between voltage and current in a pure inductive circuit. 3
- 7. When a voltage of $(100+j60)$ V is applied to a circuit, a current of $(3+j6)$ A is flowing. Find the average power consumed in the circuit. 3
- 8. Compare series and parallel resonant circuits in any three aspects. 3
- 9. What are the basic features of a balanced 3ϕ system? 3
- 10. List out any three advantages of poly-phase system over single-phase system. 3

PART—B

20×2=40

Instructions : (1) Answer *any five* questions.
 (2) Each question carries **ten** marks.
 (3) Answers should be comprehensive and the criterion for valuation is the content but not the length of the answer.

- 11. (a) Derive an equation for transformation of star-connected resistances into delta-connected resistances. 5
- (b) A network of resistors is shown in Fig. 1. Find the resistance between the terminals A and B by using star/delta transformation. 5

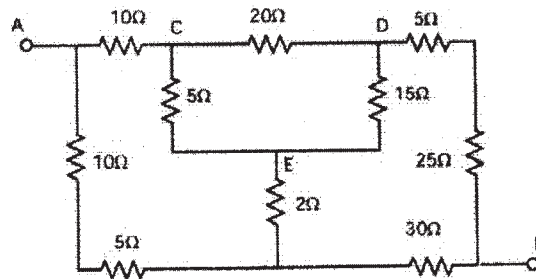


Fig. 1

- * **12.** Find the current through $4\ \Omega$ resistor of the circuit shown in Fig. 2 by using Kirchoff's laws. Also find the total current supplied by the voltage source. 8+2

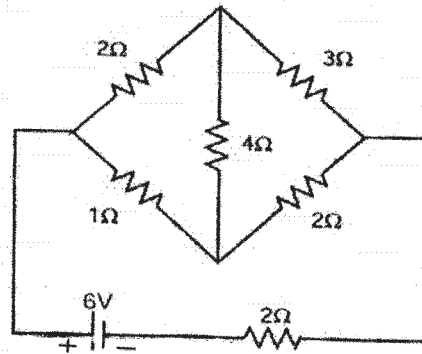


Fig. 2

- 13.** (a) Convert the given current source (Fig. 3) into voltage source. 3

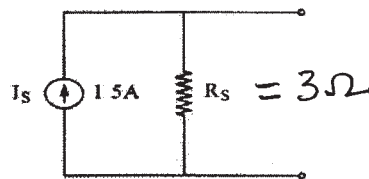


Fig. 3

- (b) Find the current through $12\ \text{ohm}$ resistor for the circuit shown in Fig. 4 by using superposition theorem. 8

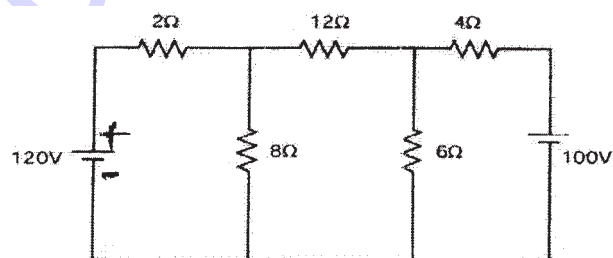


Fig. 4

- * **14.** (a) Derive the formula for average value of sinusoidal current wave by using analytical method. 4

- (b) A sinusoidal current wave is given by $i = 100 \sin 100\pi t$. Determine (i) the average value (ii) RMS value (iii) form factor (iv) peak factor. 2+2+1+1

- * **15.** (a) Derive the relation between voltage and current in a pure capacitive circuit. 4
- (b) A coil takes a current of 5 A from a 20 V d.c. supply. When connected to a 200 V, 50 Hz a.c. supply, the current is 25 A. Calculate (i) resistance (ii) inductance (iii) impedance of the coil, and power factor of the circuit. Also draw the relevant phasor diagram. 4+2
- 16.** (a) Define resonant frequency and derive the formula for resonant frequency of an RLC series. 4
- (b) Find total impedance, line current, voltage across each and power factor for a series circuit, consisting of a coil of inductance 0.1 H, resistance 8 Ω and a capacitance of 120 μF connected to a 250 V, 50 Hz supply. 6
- 17.** (a) An inductive coil of resistance 20 ohms and inductance 0.01 H is connected to a 200 V, 50 Hz supply. What capacitance placed in parallel will produce resonance? Also find the total current taken from the supply. 4
- (b) A coil of resistance 50 Ω and inductance 318 mH is connected in parallel with a circuit consisting of a 75 Ω resistor in series with a 159 μF capacitor. The circuit is connected to a 230 V, 50 Hz supply. Determine the supply current and power factor of the circuit. 6
- 18.** (a) Define polyphase circuit. Draw graphically 3-phase waveforms and write their e.m.f. equations induced in three phases. 5
- (b) Three similar coils each having an impedance of $(8 + j6)$ ohm are connected in star to a 3-ph 400 V supply. Find the line current, power and power factor. If two wattmeters are used to measure power, calculate the reading of two wattmeters. 5
