



C14-EE-305

4247

**BOARD DIPLOMA EXAMINATION, (C-14)  
SEPTEMBER/OCTOBER - 2020  
DEEE—THIRD SEMESTER EXAMINATION**

ELECTRONICS—I

Time : 3 hours ]

[ Total Marks : 80

---

**PART—A**

3×10=30

**Instructions** : (1) Answer **all** questions.  
(2) Each question carries **three** marks.  
(3) Answers should be brief and straight to the point and shall not exceed *five* simple sentences.

1. State the properties of a resistance of a resistor.
2. Define self-inductance and mutual inductance.
3. Compare the performance characteristics of a transistor in CB and CE configurations.
4. List the different types of filters.
5. Draw Zener diode regulator circuit.
6. Draw the *V-I* characteristics of SCR.
7. List the applications of optocoupler.

- \* 8. List the causes for instability of bias in transistor amplifier.
- 9. State the necessity of biasing.
- 10. Classify amplifiers based on number of stages.

**PART—B**

10×5=50

**Instructions :** (1) Answer *any five* questions.

(2) Each question carries **ten** marks.

(3) Answers should be comprehensive and the criterion for valuation is the content but not the length of the answer.

- 11. (a) Compare the features of carbon and wirewound potentiometers. 5
- (b) List the factors affecting the value of capacitance of a capacitor. 5
- 12. Explain the formation of *N-P-N* transistor with a neat sketch.
- 13. Draw the circuit of full-wave bridge rectifier and explain its working.
- 14. Explain the working of phototransistor and draw its *V-I* characteristics.
- 15. Explain the construction of solar cell and its working.
- 16. Draw the circuit of transistor amplifier circuit and explain its operation.
- 17. Draw the circuit of transformer coupled CE amplifier and explain its working.
- \* 18. (a) Define bandwidth and gain in terms of decibel. 4
- (b) Draw the frequency response of RC coupled amplifier and indicate the gain, bandwidth, upper cut-off and lower cut-off frequencies. 6

\*\*\*