

4247

**BOARD DIPLOMA EXAMINATION, (C-14)
MARCH/APRIL-2019
DEEE – THIRD SEMESTER EXAMINATION**

ELECTRONICS - I

Time:3 Hours

Max.Marks:80

PART-A**10x3=30M**

Instructions: 1) Answer **all** questions. Each question carries **3** marks.
2) Answer should be brief and straight to the point and shall not exceed **five** simple sentences.

- 1) Define capacitance and list its specification.
- 2) Define self inductance and mutual inductance.
- 3) Distinguish between intrinsic and extrinsic semiconductors.
- 4) List advantages of Bridge rectifier.
- 5) List different types of filters.
- 6) What is the principle of photodiode?
- 7) List the applications of solar cell.
- 8) List causes for instability of transistor biasing.
- 9) Define operating point.
- 10) Define gain interms of decibel.

PART-B

*

5x10=50M

- Instructions:** 1) Answer any **five** questions. Each question carries **ten** marks.
2) The answer should be comprehensive and the criteria for valuation is the content but not the length of the answer.
- 11) Explain how resistance value is calculated using colour code. Find the value of resistance with colour code yellow-violet-orange and gold.
 - 12) Explain input and output characteristics of transistor in CE configuration.
 - 13) Explain the function of Zener diode as a voltage regulator in power supply.
 - 14) Explain the construction and working of FET.
 - 15) Explain the construction and working of opto-coupler and list its applications.
 - 16) Explain the operation of transistor as an amplifier.
 - 17) Briefly give the classification of amplifiers.
 - 18) Explain the working of RC coupled CE amplifier with neat circuit diagram.

* * *

*