



C14-EE-505

4640

BOARD DIPLOMA EXAMINATION, (C-14)
OCT/NOV—2016
DEEE—FIFTH SEMESTER EXAMINATION
DIGITAL ELECTRONICS

Time : 3 hours]

[Total Marks : 80

PART—A

3×10=30

Instructions : (1) Answer **all** questions.
(2) Each question carries **three** marks.
(3) Answers should be brief and straight to the point and shall not exceed *five* simple sentences.

1. Distinguish between weighted and unweighted codes.
2. Draw the symbols of the following two-input logic gates :
 - (a) AND
 - (b) OR
 - (c) NAND
3. Compare between the TTL, CMOS and ECL logic families.
4. List any three IC numbers of two-input digital IC logic gates.
5. Define the following characteristics of digital ICs :
 - (a) Fan-out
 - (b) Noise margin
6. Draw the full-adder using two half-adders and OR gate.

- * 7. Compare the performance of serial adder with parallel adder.
- 8. State the need of preset and clear inputs of flip-flops.
- 9. Draw the NAND latch and write its truth table.
- 10. Distinguish between RAM and ROM.

PART—B

10×5=50

Instructions : (1) Answer *any five* questions.
 (2) Each question carries **ten** marks.
 (3) Answers should be comprehensive and the criterion for valuation is the content but not the length of the answer.

- 11. (a) Briefly explain the significance of parity bit. 3
- (b) Subtract the 45_{10} from 52_{10} using 2's complement method. 4
- (c) Simplify the logic expression $Y = A\bar{B} + \bar{A}B$. 3
- 12. Draw and explain CMOS NAND gate. 10
- 13. Draw and explain TTL NAND gate with open collector. 10
- 14. Draw and explain the decimal to BCD encoder. 10
- 15. (a) List any three applications of decoders. 3
- (b) Draw and explain the operation of 4×1 multiplexer. 7
- 16. (a) Distinguish between synchronous and asynchronous counters. 3
- (b) Draw and explain clocked S-R flip-flop using NAND gates. 7
- 17. Draw and explain 4-bit asynchronous counter. 10
- 18. (a) Draw and explain the basic principle of working of diode ROM. 6
- (b) Distinguish between EEPROM and UVROM. 4
