

## 6444

# BOARD DIPLOMA EXAMINATION, (C-16) JANUARY/FEBRUARY—2022

### **DEEE - FOURTH SEMESTER EXAMINATION**

ELECTRONICS ENGINEERING - II

Time: 3 hours [ Total Marks: 80

#### PART—A

 $3 \times 10 = 30$ 

**Instructions:** (1) Answer **all** questions.

- (2) Each question carries **three** marks.
- (3) Answers should be brief and straight to the point and shall not exceed five simple sentences.
- 1. Classify different types of oscillators.
- **2.** State the need for AF oscillators.
- **3.** List the advantages of ICs over discrete circuits.
- **4.** Draw the pin diagram of 555 IC.
- **5.** Define modulation and demodulation.
- **6.** Define modulation index of AM wave.
- **7.** State the advantages of electronic instruments.
- **8.** State the need for A/D converters.
- **9.** State the need of transducer in measurement systems.
- **10.** List the applications of sensors.

**1** [ Contd...

## PART—B

Instructions:		(1)	Answer any <b>five</b> questions.	
		(2)	Each question carries <b>ten</b> marks.	
		(3)	Answers should be comprehensive and criterion for valuation is the content but not the length of the answer.	ı
11.	Explain t diagram.		working of RC phase shift oscillator with the help of circuit	10
12.	• (a) Draw the circuit diagram of Hartley oscillator.			5
	(b) State the need for square wave oscillator.			5
13.	Explain the working of operational amplifier with the help of a block diagram.			10
14.	Explain the working of astable multivibrator using 555 IC and draw output waveforms.			10
15.	(a) Draw	v th	ne waveforms of amplitude modulated wave.	5
	(b) Expla	ain	the generation of sidebands.	5
16.	Explain t diagram.		functions of various stages of CRO with the help of block	10
17.	. /		n the use of thermocouple for the measurement of ature.	5
	(b) Expla	ain	about semiconductor sensors.	5
18.	Explain the construction and working of LVDT.			

