6636

BOARD DIPLOMA EXAMINATIONS

OCT/NOV-2019

DEEE- FIFTH SEMESTER

POWER ELECTRONICS & PLC

Time: 3 hours Max. Marks: 80

PAŘŤ – A

 $3 \times 10 = 30$

Instructions:

- 1. Answer all questions.
- 2. Each question carries Three Marks.
- 3. Answer should be brief and straight to the point and should not exceed five simple sentences.
- 1. State the need of commutation in SCR.
- 2. State any six rating of SCR.
- 3. Classify the converters.

4.

- 4. Define an inverter and state any four applications.
- \$\forall 5. State any six applications of Cyclo Convertors.
 - 6. List any three devices used to suppress spikes in supply system.
- 7. State the factors affecting the speed of DC motor.
- 8. Define automation and state its any two advantages.
- 9. Draw the ladder diagram for logic NAND gate.
- 10. State any three advantages of PLC.

- **Instructions**: 1. Answer any **Five** questions
 - Each question carries **TEN** Marks.
 - 3. Answer should be comprehensive and criteria for valuation are the content but not the length of the answer.
- 11. (a) Explain the working of SCR in forward and Reserve bias modes.
 - (b) List any five applications of SCR.
- 12. (a) Explain auxiliary commutation of SER with the help of Circuit diagram.
 - (b) Draw the V I characteristics of TRIAC.
- 13. Explain the working of single phase fully controlled Converter under resistive load with neat wave forms.
- 14. (a) Explain briefly the control methods of chopper.
 - (b) Explain the basic operating principle of Cyclo converter.
- (a) Explain the operation of light dimmer circuit using DIAC **%** TRIAC with neat sketch.
 - (b) Explain the operation of Burglar Alarm Circuit using SCR With neat sketch.
- 16. (a) Explain the closed loop system of Water level controller.
 - (b) State any five advantages of automation.
- 17. (a) Compare open loop and closed loop control systems in five Aspects.
 - (b) Explain the ON delay timer (Ton) instruction.
- 18. Draw and explain the ladder diagram of DOL starter.