

6637

## BOARD DIPLOMA EXAMINATION

SEPTEMBER/OCTOBER-2020

DEEE – FIFTH SEMESTER

DIGITAL ELECTRONICS &amp; MICROCONTROLLERS

Time: 3 hours

Max. Marks: 80

PART – A

3 X 10 = 30

- Instructions:**
1. Answer **all** questions.
  2. Each question carries **Three** Marks.
  3. Answer should be brief and straight to the point and should not exceed five simple sentences.

1. Perform the following subtraction using 2's complement method.
  - a)  $(1101)_2 - (0110)_2$
  - b)  $(1010)_2 - (1000)_2$
2. Draw the symbols of basic gates and write their truth table.
3. Construct full adder circuit using two half adders and an OR gate.
4. Compare Serial adder and parallel adder.
5. State the need of preset and clear inputs of Flip- Flops.
6. State the need of a register. Write types of registers.
7. List any three commonly used commercial Microcontroller device families.
8. Draw the pin diagram of 8051 Microcontroller.
9. List any three logic instructions of 8051 Microcontroller.
10. Mention different addressing modes of 8051 Microcontroller.

[Cont..]

**PART – B**

**5 X 10 = 50**

- Instructions:**
1. Answer any **Five** questions
  2. Each question carries **TEN** Marks.
  3. Answer should be comprehensive and criteria for valuation is the content but not the length of the answer.

11. Draw and explain TTL NAND gate with totem pole output. 10M
12. Draw and explain a 4-bit parallel adder using full-adders. 10M
13. a) Explain the working of serial adder with block diagram. 5M  
b) Explain 3 x 8 Decoder along with its truth table. 5M
14. Draw the explain 4-bit synchronous Counter. 10M
15. a) Draw and explain 4-bit shift left register. 6M  
b) Classify various types of memories. 4M
16. Draw the block diagram of 8051 Microcontroller and explain the functions of each block. 10M
17. Mention the major groups in the instruction set of 8051 Microcontroller and explain each group with examples. 10M
18. a) Write a program to add two 8-bit numbers. 5M  
b) Write a program to multiply two 8-bit numbers. 5M