C16-EE-505

## 6637

# **BOARD DIPLOMA EXAMINATION, (C-16)**

# JANUARY/FEBRUARY—2022

#### **DEEE - FIFTH SEMESTER EXAMINATION**

#### DIGITAL ELECTRONICS AND MICROCONTROLLERS

Time: 3 hours ] [ Total Marks: 80

#### PART—A

 $3 \times 10 = 30$ 

**Instructions:** 

- (1) Answer **all** questions.
  - (2) Each question carries **three** marks.
  - (3) Answers should be brief and straight to the point and shall not exceed five simple sentences.
- 1. Convert the following numbers into decimal:

(a)  $(11011)_2$  (b)  $(22.70)_8$ 

(c) (2BD)<sub>16</sub>

- 2. Define Fan-in and Fan-out capacity of a digital IC.
- 3. Mention any three applications of a Multiplexer.
- 4. Draw the logic diagram of 1-Bit comparator and write its truth table.
- 5. State the necessity of Clock in Flip-Flops. Mention the types of triggering in Flip-Flop.
- 6. Distinguish between Synchronous and Asynchronous counters.
- 7. Mention any six types of Registers used in 8051 Microcontroller.
- State the alternate function of part-3 of 8051 Microcontroller. 8.

- **9.** Give the different between Machine level and Assembly level programming.
- **10.** List any three Arithmetic instructions of 8051 with examples.

### **PART—B** 10×5=50

**Instructions:** (1) Answer any **five** questions.

- (2) Each question carries **ten** marks.
- (3) Answers should be comprehensive and criterion for valuation is the content but not the length of the answer.
- **11.** (a) Perform the subtraction of binary numbers using 2's complement method:
  - (i)  $(101011)_2 (11001)_2$ (ii)  $(100100)_2 - (100011)_2$

5

(b) Compare the TTL, CMOS and ECL logic families.

5

**12.** Explain 2's Complement parallel Adder/Subtractor circuit.

10

**13.** (a) Draw and explain BCD to Decimal Decoder.

5 5

(b) Draw and explain 4×1 multiplexer.

10

**14.** Explain the working of Master Slave JK Flip-Flop circuit with necessary diagrams.

10

**15.** Draw and explain the working of 4-bit bi-directional shift register.

10

**16.** Explain the 8051 Microcontroller pin configuration and specify the purpose of each pin.

**17.** (a) Explain Unconditional and Conditional jump instructions in 8051 Microcontroller.

5

(b) Define subroutine and explain its use.

5

/6637

2

**18.** (a) Write a program to add two 8-bit numbers stored in memory 2400H and 2401H. Store the result in 2402H and 2403H.

5

(b) Explain the terms operation code and operand instructions with example.

5

 $\star\star\star$ 

