



C09-IT-304

3302

BOARD DIPLOMA EXAMINATION, (C-09)

MARCH/APRIL—2014

DIT—THIRD SEMESTER EXAMINATION

DIGITAL ELECTRONICS AND COMPUTER ARCHITECTURE

Time : 3 hours]

[Total Marks : 80

PART—A

3×10=30

Instructions : (1) Answer **all** questions.

(2) Each question carries **three** marks.

(3) Answers should be brief and straight to the point and shall not exceed *five* simple sentences.

1. Draw the symbols and truth tables for the following gates :

(a) AND

(b) OR

2. Express the Boolean function $F = A \bar{B}C$ in a sum of minterms and product of maxterms.

3. Draw the NOR latch and write its truth table.

4. List the applications of counters.

5. What is a demultiplexer?

6. Define execution cycle.

7. State the basic types of information representation in a computer.

- * 8. Explain one address instruction with an example.
9. Distinguish between physical address space and logical address space.
10. Define polling.

PART—B

10×5=50

Instructions : (1) Answer *any five* questions.

(2) Each question carries **ten** marks.

(3) Answers should be comprehensive and the criterion for valuation is the content but not the length of the answer.

11. Draw and explain digital comparator for two 4-bit binary numbers.
12. Explain the principle of operation of monostable multivibrator circuit.
13. Explain the asynchronous decade counter with diagram.
14. Draw the block diagram of a digital computer and explain the function of each unit.
15. Draw and explain the flowchart for the sequence of operations for subtraction of floating-point numbers.
16. Explain synchronous and asynchronous data transfer.
17. (a) Draw and explain a serial in parallel out register.
(b) Explain the 4×1 multiplexer with diagram.
- * 18. (a) Explain the sequence of operations for addition and subtraction of fixed point numbers.
(b) What is meant by memory hierarchy? State its need.
