



C09-CM-304/C09-IT-304

3230

BOARD DIPLOMA EXAMINATION, (C-09)
OCT/NOV—2016
DCME—THIRD SEMESTER EXAMINATION

DIGITAL ELECTRONICS AND COMPUTER ARCHITECTURE

Time : 3 hours]

[Total Marks : 80

PART—A

3×10=30

- Instructions :** (1) Answer **all** questions.
(2) Each question carries **three** marks.
(3) Answers should be brief and straight to the point and shall not exceed *five* simple sentences.

1. Draw the symbols and truth tables for the following gates :
2×1½=3
 - (a) AND
 - (b) OR
2. State De Morgan's theorems. 2×1½=3
3. Draw the NOR latch and write its truth table. 2×1½=3
4. List the applications of counters. 1×3=3
5. Define the following : 2×1½=3
 - (a) Multiplexer
 - (b) Decoder
6. Define instruction cycle. 3
7. Define floating point representation of numbers. 3

- * 8. What is the difference between register addressing mode and register indirect addressing mode? 3
9. Distinguish between main memory and auxiliary memory. 3
10. What is meant by asynchronous data transfer? 3

PART—B

10×5=50

Instructions : (1) Answer *any five* questions.

(2) Each question carries **ten** marks.

(3) Answers should be comprehensive and the criterion for valuation is the content but not the length of the answer.

11. Draw and explain 2's complement adder-subtractor. 4+6=10
12. Explain the principle of operation of Schmitt trigger circuit. 4+6=10
13. Draw and explain a mod-8 ripple counter. 4+6=10
14. Draw the block diagram of a digital computer and explain the function of each unit. 4+6=10
15. Draw and explain the flowchart for multiplication of floating point numbers. 4+6=10
16. (a) Explain priority interrupt mode of data transfer. 5
- (b) Explain daisy chain priority interrupt mode of data transfer. 5
17. (a) Explain the working of parallel-in serial-out register. 5
- (b) Explain the 1 4 demultiplexer with diagram. 5
- * 18. (a) Draw the flowchart indicating sequence of operations for subtraction of fixed point numbers. 5
- (b) Explain the memory interleaving. 5
