



C09-CM-304/C09-IT-304

3230

BOARD DIPLOMA EXAMINATION, (C-09)

OCT/NOV—2017

DCME—THIRD SEMESTER EXAMINATION

DIGITAL ELECTRONICS AND COMPUTER ARCHITECTURE

Time : 3 hours]

[Total Marks : 80

PART—A

3×10=30

Instructions : (1) Answer **all** questions.

(2) Each question carries **three** marks.

(3) Answers should be brief and straight to the point and shall not exceed *five* simple sentences.

1. Draw the logic diagram for 4-bit parallel binary adder.
2. State De Morgan's theorems.
3. State the need for a master-slave flip-flop.
4. Distinguish between asynchronous and synchronous counters.
5. What is an encoder?
6. Define micro- and macrooperation.
7. Define opcode, operand and address.

- * 8. Define fixed point representation of numbers.
- 9. Write the advantages of Cache memory.
- 10. Explain the need for an interface.

PART—B

10×5=50

Instructions : (1) Answer *any five* questions.

(2) Each question carries **ten** marks.

(3) Answers should be comprehensive and the criterion for valuation is the content but not the length of the answer.

- 11. (a) Explain about AND, OR and NOT gates.
(b) Explain the operation of half-adder with logic diagram and truth table.
- 12. Draw the logic circuit, truth table and timing diagrams for a clocked D-flip-flop. Explain its operation.
- 13. Explain the operation of a ripple counter.
- 14. (a) State the use of shift register as memory.
(b) Describe the operation of a 1×4 de-multiplexer with a circuit diagram.
- 15. Draw the functional block diagram of digital computer and explain the function of each unit.
- 16. Explain floating addition and subtraction operation with flowchart.
- * 17. (a) Explain any five addressing modes.
(b) Explain associative memory.
- 18. Explain programmed I/O method of data transfer.
