Code: C16 CM/IT-302

### 6228

# **BOARD DIPLOMA EXAMINATION**

**IUNE - 2019** 

## \* DIPLOMA IN COMPUTER ENGINEERING/IINFORMATION TECHNOLOGY DIGITAL ELECTRONICS & COMPUTER ARCHITECTURE THIRD SEMESTER EXAMINATION

**Time: 3 Hours Total Marks: 80** 

#### PART - A $(3m \times 10 = 30m)$

Note 1:Answer all questions and each question carries 3 marks

- 4. Write the drawbacks of ripple counter
- 5. What is a combinational circuit? Draw the block diagram
- 6. Write the purpose of Accumulator Instruction register and program counter in Accumulator based CPU
- 7. Write about following addressing modes
  - immediate ii) indire i)
- 8. Define mantissa and exponent of floating point numbers
- 9. List different characteristics of memory devices
- 10. Define system bus. Write different buses used in computer

## $(10m \times 5 = 50m)$

Note 1:Answer any five questions and each question carries 10 marks

- 2:The answers should be comprehensive and the criteria for valuation is the content but not the length of the answer
- 11. Draw and explain operation of 4-bit 2's complement adder/subtractor
- 12. a) Write about asynchronous inputs of flip flop.
  - b) draw the block diagram of master-slave J-K flip flop
- 13. Draw and explain the operation of 3-bit asynchronous counter
- 14A. Explain the operation of 4-bit shift right register

- B. Explain the operation of 1X4 de multiplexer
- 15. Write about the following
  - a) Stored program concept b) Instruction cycle
- 16. Explain zero address, one address, two address and three address instructions with simple example
- A.A.H.M. & V.V.R.S.R. POLYTEINIC, GUDLAVALLERU, KRISHMA DIST. A.P. 17A. Explain floating point multiplication operation with flowchart
  - B. Explain cache memory organization
  - 18. Explain in detail DMA control data transfer

Page: 2 of 2