

6228
BOARD DIPLOMA EXAMINATION
JUNE - 2019

*** DIPLOMA IN COMPUTER ENGINEERING/INFORMATION TECHNOLOGY**
DIGITAL ELECTRONICS & COMPUTER ARCHITECTURE
THIRD SEMESTER EXAMINATION

Time: 3 Hours

Total Marks: 80

PART - A (3m x 10 = 30m)

Note 1: Answer all questions and each question carries 3 marks

2: Answers should be brief and straight to the point and shall not exceed 5 simple sentences

1. Minimise the following Boolean function using K-Map
 $F(w,x,y) = \sum m(1,2,3,5,6,7)$
2. Draw the symbols and truth tables for following gates:
 a) EX-OR b) EX-NOR
3. what is the use of binary cell
4. Write the drawbacks of ripple counter
5. What is a combinational circuit? Draw the block diagram
6. Write the purpose of Accumulator, Instruction register and program counter in Accumulator based CPU
7. Write about following addressing modes
 i) immediate ii) indirect
8. Define mantissa and exponent of floating point numbers
9. List different characteristics of memory devices
10. Define system bus. Write different buses used in computer

PART - B (10m x 5 = 50m)

Note 1: Answer any five questions and each question carries 10 marks

2: The answers should be comprehensive and the criteria for valuation is the content but not the length of the answer

- *
11. Draw and explain operation of 4-bit 2's complement adder/subtractor
 12. a) Write about asynchronous inputs of flip flop.
 b) draw the block diagram of master-slave J-K flip flop
 13. Draw and explain the operation of 3-bit asynchronous counter
 - 14A. Explain the operation of 4-bit shift right register

B. Explain the operation of 1X4 de multiplexer

15. Write about the following

a) Stored program concept b) Instruction cycle

*

16. Explain zero address, one address, two address and three address instructions with simple example

17A. Explain floating point multiplication operation with flowchart

B. Explain cache memory organization

18. Explain in detail DMA control data transfer

- xxx -

030 030 030 030 030

*

*