



C16-CM-302/C16-IT-302

6228

BOARD DIPLOMA EXAMINATION, (C-16)

OCT/NOV—2017

DCME—THIRD SEMESTER EXAMINATION

DIGITAL ELECTRONICS AND COMPUTER ARCHITECTURE

Time : 3 hours]

[Total Marks : 80

PART—A

10×3=30

Instructions : (1) Answer **all** questions.

(2) Each question carries **three** marks.

(3) Answers should be brief and straight to the point and shall not exceed *five* simple sentences.

1. Define Exclusive OR gate. Give its truth table
2. State DeMorgan's laws
3. Write differences between edge triggering and level triggering in flip flops.
4. State the applications of counters.
5. Define multiplexer. Give block diagram of 2×1 multiplexer.
6. Draw the block diagram of digital computer.
7. What are operand, opcode and address?

- * 8. Differentiate between register and register indirect addressing modes.
9. List various memory device characteristics.
10. What is interrupt initiated I/O?

PART—B

5×10=50

Instructions : (1) Answer *any five* questions.

(2) Each question carries **ten** marks.

(3) Answers should be comprehensive and the criterion for valuation is the content but not the length of the answer.

11. Explain the operation of 4-bit digital comparator.
12. Implement RS latch using NAND and NOR gates and explain with truth tables.
13. Explain the working of serial in serial out and serial in parallel out registers.
14. (a) Write about 4-bit ring counter. 5
 (b) What is decoder? Explain with an example 5
15. Explain sequential execution of program stored in memory by CPU
16. Explain fixed point multiplication with an example
17. (a) Write about principle and advantage of cache memory. 5
 (b) Give two address instruction for $(A+B)*(C+D)$ 5
18. Explain in detail about DMA controlled data transfer.
